

CS2310  
FUNDAMENTALS OF COMPUTER DESIGNING

AKSHITHA (CS22B019), ANJALI (CS22B046)

November 14, 2023



# Contents

<b>1</b>	<b>ARCHITECTURE</b>	<b>3</b>
1.1	GENERAL CPU REGISTER . . . . .	3
1.2	INSTRUCTION REGISTER . . . . .	4
1.3	MEMORY ADDRESS REGISTER . . . . .	4
1.4	PROGRAM COUNTER . . . . .	5
1.5	ARITHMETIC AND LOGICAL UNIT . . . . .	6
1.6	STATUS REGISTER . . . . .	6
<b>2</b>	<b>INSTRUCTION SET</b>	<b>7</b>
2.1	NOP . . . . .	7
2.2	LDA . . . . .	8
2.3	STA . . . . .	8
2.4	ADD . . . . .	9
2.5	SUB . . . . .	9
2.6	LDI . . . . .	10
2.7	JMP . . . . .	10
2.8	SWAP . . . . .	10
2.9	JNZ . . . . .	11
2.10	MOVAC . . . . .	11
<b>3</b>	<b>ASSEMBLY PROGRAMS</b>	<b>11</b>
<b>4</b>	<b>MICROINSTRUCTIONS AND CONTROLLER LOGIC DESIGN</b>	<b>13</b>
4.1	NOP . . . . .	13
4.2	LDA . . . . .	13
4.3	STA . . . . .	13
4.4	ADD . . . . .	14
4.5	SUB . . . . .	14
4.6	JMP . . . . .	14
4.7	SWAP . . . . .	14
4.8	JNZ . . . . .	15
4.9	MOVAC . . . . .	15
4.10	MOVAC . . . . .	15
4.11	MOVBA . . . . .	15
4.12	MOVCB . . . . .	16
4.13	MOVAB . . . . .	16
4.14	MOVCA . . . . .	16
4.15	MOVBC . . . . .	16
4.16	HLT . . . . .	17
<b>5</b>	<b>SYSTEM RESET</b>	<b>17</b>

# 1 ARCHITECTURE

Gajendra-1 represents a computer system characterized by a bus-organized architecture. In this design, a common pathway known as bus, is employed to efficiently manage the exchange of both data and instructions among various components within the circuit.


The layout of the circuit is shown below and let's look into the components in detail:

Internal components of the gajendra-1:

- GENERAL CPU REGISTER
- INSTRUCTION REGISTER
- MEMORY ADDRESS REGISTER
- PROGRAM COUNTER
- ARITHMETIC AND LOGICAL UNIT
- STATUS REGISTER

 
## 1.1 GENERAL CPU REGISTER

A register is normally used for temporary storage of a related set of bits for some operation. An 8-bit-register is constructed by integrating eight D-flipflops, all synchronized by a common clock. Additionally, eight tri-state buffers are employed in conjunction with the register. When REG\_IN is set to 1, the register acquires an 8-bit input, DATA\_IN, from the common bus. REG\_OUT serves as an enable for tri-state buffer, regulating the output (OUT) that the register provides back to the bus. Simultaneously, the output of the register, contained in the DISP, is not subjected to external control.



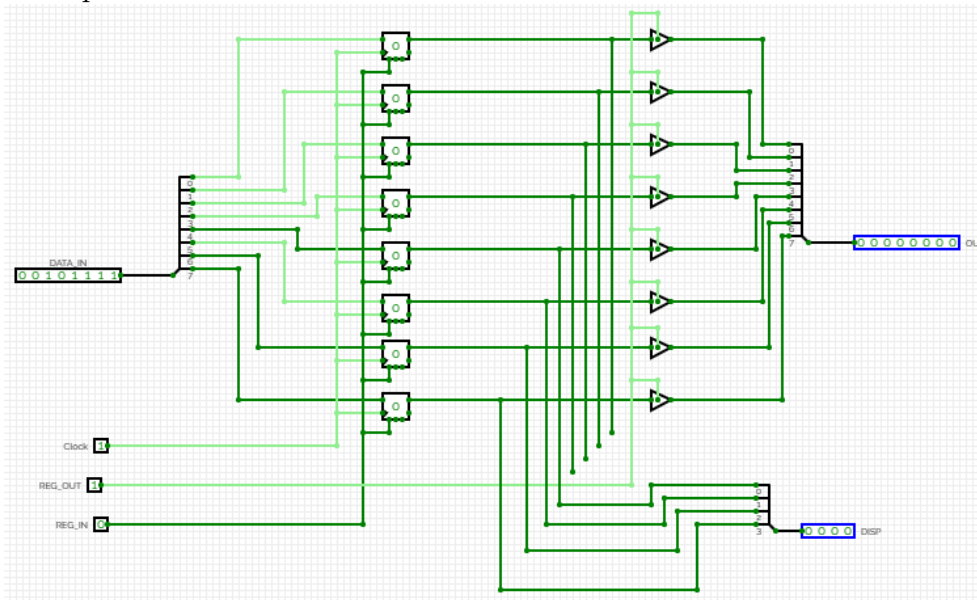
## 1.2 INSTRUCTION REGISTER

The instruction register (IR) serves as a temporary repository for the current instruction throughout its execution. This register receives its input, denoted as DATA\_IN, from the common bus under the control of the REG\_IN signal. The initial four bits of this input explicitly define the instruction to be carried out. The DISP output conveys these initial four bits to the control logic, providing the necessary instruction for the completion of the current operation.


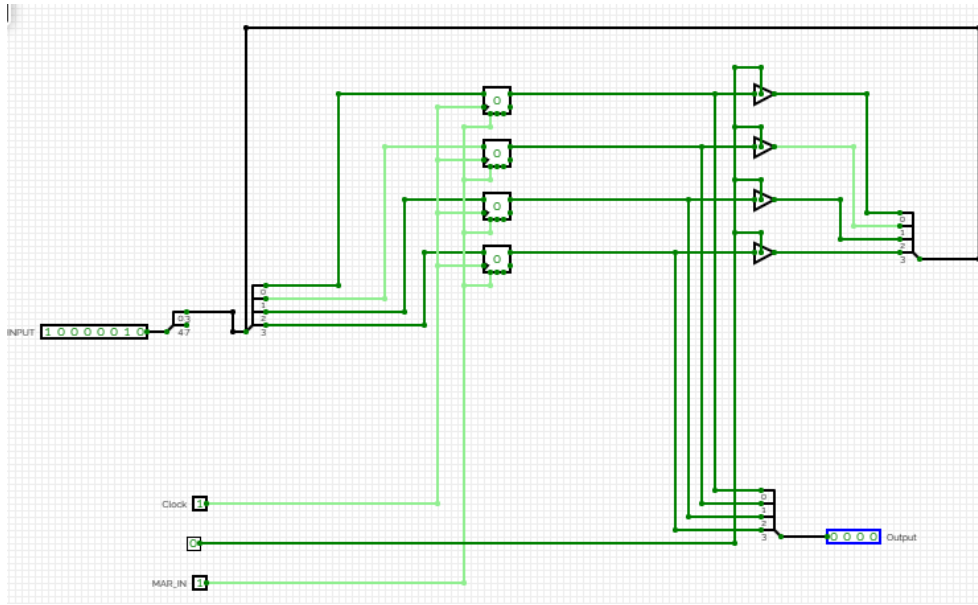
## 1.3 MEMORY ADDRESS REGISTER

Memory Address Register (MAR) functions as a pivotal element in the memory access process. Its job is to remember the address of the specific spot in memory we want to read. It sends this address to the RAM using a 4-bit output known as Output. The program counter address smoothly transfers into the Memory Address Register (MAR) by means of Input when MAR\_IN is set to 1.




## 1.4 PROGRAM COUNTER

The program is initially stored at the outset of memory, with the first instruction residing at binary address 0000, the second at address 0001, and so on. The program counter is instrumental in this process, as it systematically increments from 0000 to 1111, serving the crucial role of transmitting the address of the next instruction to be fetched and executed from memory.


Control inputs of PC:

- **INC:** Increments the count by one given a clock pulse.
- **LOAD:** The PC will be loaded with the values available in the common bus. We consider the least significant 4-bits as the address.
- **OUT:** The PC's current count value will be output to the bus. Again, we note that only 4-bits are important- the additionally most significant 4-bits will be ignored by the rest of the circuitry.
- **RESET:** Resets the PC count value to zero.

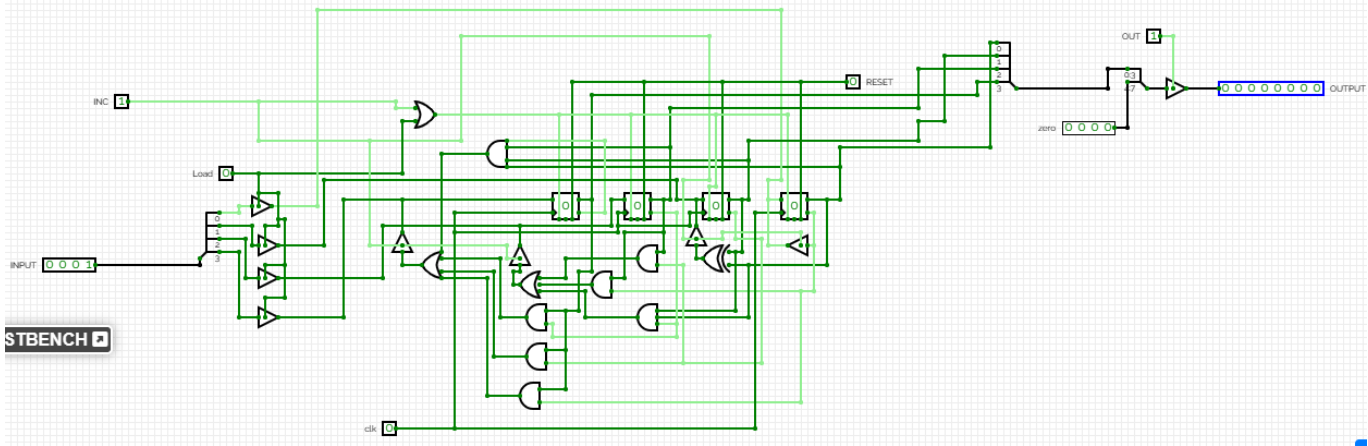
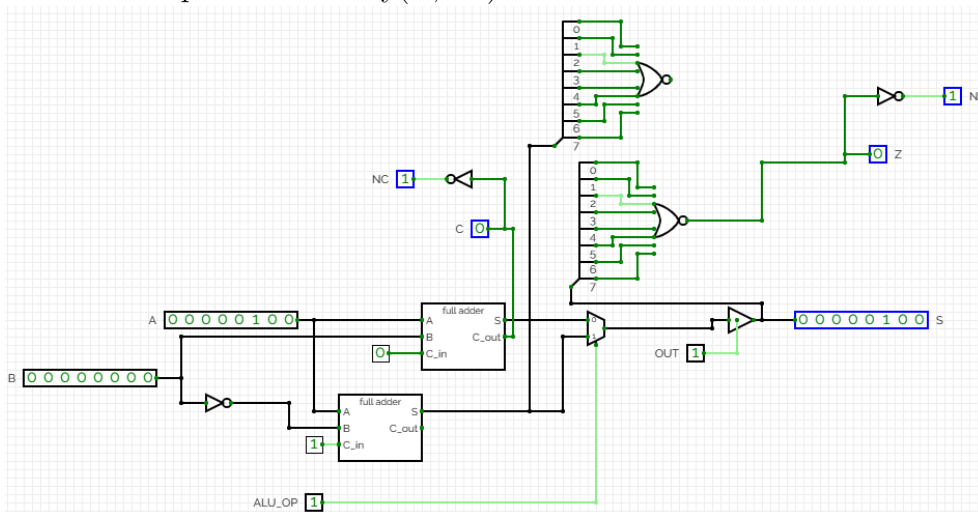
## 1.5 ARITHMETIC AND LOGICAL UNIT


The Arithmetic Logic Unit (ALU) is responsible for executing both addition and subtraction operations. The ALU operates based on the value of  $ALU\_OP$ : when  $ALU\_OP$  is 1, it performs  $A - B$ , and when it's 0, the operation is  $A + B$ . When the  $OUT$  signal is set to 1, the ALU writes the result ( $S$ ) to the common bus. The ALU is asynchronous, meaning its output changes immediately upon any alteration in its inputs. Additionally, the ALU is equipped to determine whether any of its operations result in a zero output ( $Z, NZ$ ). It also provides the output of the carry ( $C, NC$ ).


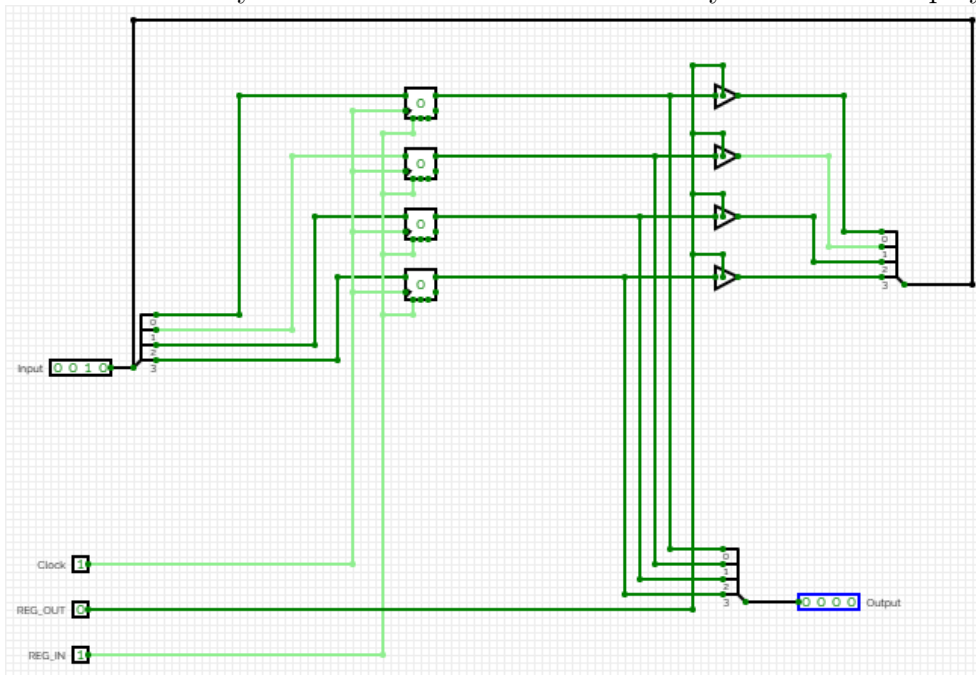
## 1.6 STATUS REGISTER

Status Register is a 4-bit register which stores essential flags denoted as  $C$  (Carry),  $NC$  (No Carry),  $Z$  (Zero), and  $NZ$  (Not Zero). Upon the ALU writing its output to the common bus, the Status Register takes its input from the ALU, and the resulting flags are displayed. This is done by connecting the  $REG\_IN$  directly to the  $OUT$  of ALU. This configuration ensures

that the status of key arithmetic conditions is efficiently stored and displayed.



## 2 INSTRUCTION SET

We define our own instruction set. We assign specific machine codes for each instruction. The operation bits from the opcode needs to be passed from the instruction register (IR) to the controller to interpret what instruction needs to be executed.

Note that if K is the address then  $[K]$  denotes the value at the address.

### 2.1 NOP

#### NOP

##### **Description:**

The instruction performs no operation and increments the program counter.

##### **Operation:**

(i) No

##### **Syntax:**

(i) *NOP*

##### **Operands:**

None

##### **Program counter:**

$PC \leftarrow PC + 1$

##### **8-bit Opcode:**

0000	XXXX
------	------

## 2.2 LDA

**Description:**

Loads value from the given address into the Accumulator(REG\_A)

**Operation:**

- (i)  $R_A \leftarrow [K]$

**Syntax:**

- (i) *LDA K*

**Operands:**

$$0 \leq K \leq 15$$

**Program counter:**

$$PC \leftarrow PC + 1$$

**8-bit Opcode:**

0001	$0xK(XXXX)$
------	-------------

## 2.3 STA

**Description:**

Stores value from the Accumulator(REG\_A) into the given address.

**Operation:**

- (i)  $[K] \leftarrow R_A$

**Syntax:**

- (i) *STA K*

**Operands:**

$$0 \leq K \leq 15$$

**Program counter:**

$$PC \leftarrow PC + 1$$

**8-bit Opcode:**

0010	$0xK(XXXX)$
------	-------------



## 2.4 ADD

**Description:**

It updates the value stored in the accumulator by adding the value stored in the given location to the value stored in it.

**Operation:**

- (i)  $(i)R_B \leftarrow [K]$
- (ii)  $R_A \leftarrow R_A + R_B$

**Syntax:**

(i) *ADD K*

**Operands:**

$0 \leq K \leq 15$

**Program counter:**

$PC \leftarrow PC + 1$

**8-bit Opcode:**

0011	$0xK(XXXX)$
------	-------------

## 2.5 SUB

**Description:**

It updates the value stored in accumulator by subtracting the value stored in the given location to the value stored in it

**Operation:**

- (i)  $(i)R_B \leftarrow [K]$
- (ii)  $R_A \leftarrow R_A - R_B$

**Syntax:**

(i) *SUB K*

**Operands:**

$0 \leq K \leq 15$

**Program counter:**

$PC \leftarrow PC + 1$

**8-bit Opcode:**

0100	$0xK(XXXX)$
------	-------------

## 2.6 LDI

**Description:**

Loads a 4-bit constant value directly to the accumulator.

**Operation:**

- (i)  $R_A \leftarrow K$

**Syntax:**

- (i) *LDI K*

**Operands:**

$$0 \leq K \leq 15$$

**Program counter:**

$$PC \leftarrow PC + 1$$

**8-bit Opcode:**

0101	$K(XXXX)$
------	-----------

## 2.7 JMP

**Description:**

The program counter jumps to the given 4-bit address unconditionally.

**Operation:**

- (i)  $PC \leftarrow K$

**Syntax:**

- (i) *JMP K*

**Operands:**

$$0 \leq K \leq 15$$

**Program counter:**

$$PC \leftarrow K$$

**8-bit Opcode:**

0110	$0xK(XXXX)$
------	-------------

## 2.8 SWAP

**Description:**

Swaps the values present in REG\_A and REG\_C using temporary register (i.e. REG\_B).

**Operation:**

- (i)  $R_B \leftarrow R_A$   
(ii)  $R_A \leftarrow R_C$   
(iii)  $R_C \leftarrow R_B$

**Syntax:**

- (i) *SWAP*

**Operands:**

—

**Program counter:**

$$PC \leftarrow PC + 1$$

**8-bit Opcode:**

0111	$XXXX$
------	--------

## 2.9 JNZ

**Description:**

The program counter jumps to the given 4-bit address if the value of ALU\_OUT is non zero.

**Operation:**

(i)  $PC \leftarrow K$

**Syntax:**

(i)  $JNZ\ K$

**Operands:**

$0 \leq K \leq 15$

**Program counter:**

$PC \leftarrow K$

**8-bit Opcode:**

1000	$0xK(XXXX)$
------	-------------

## 2.10 MOVAC

**Description:**

Copy the values present in REG\_A to REG\_C, the value in REG\_A remains unchanged.

**Operation:**

(i)  $R_C \leftarrow R_A$

**Syntax:**

(i)  $MOVAC$

**Operands:**

—

**Program counter:**

$PC \leftarrow PC + 1$

**8-bit Opcode:**

1001	$XXXX$
------	--------

## 3 ASSEMBLY PROGRAMS

### EXAMPLE 1

Adding two numbers ( $A, B$ ):

Let the values of  $A, B$  be stored at locations  $0xC$  and  $0xD$  respectively.

Address	Assembly code	Machine Code
$0x0$	LDA $0xC$	$0x1C$
$0x1$	ADD $0xD$	$0x3D$
$0x2$	MOVAC	$0x90$

### EXAMPLE 2

Adding and subtracting 4 numbers in some combination:

Let  $E = A + B - C + D$

The values of  $A, B, C, D, E$  be stored at locations  $0xC, 0xD, 0xE, 0xF$  and  $0xB$  respectively.

Address	Assembly code	Machine Code
0x0	LDA 0xC	0x1C
0x1	ADD 0xD	0x3D
0x2	SUB 0xE	0x4E
0x3	ADD 0xF	0x3F
0x4	STA 0xB	0x2B

### EXAMPLE 3


Multiplication using repeated addition:

Say we want to perform  $a * b$ .

Let the values of  $a, b, 1$  be stored at the locations  $0xF, 0xE, 0xD$ .

Address	Assembly code	Machine Code
0x0	LDA 0xF	0x1F
0x1	MOVAC	0x90
0x2	LDI 0	0x50
0x3	ADD 0xE	0x3E
0x4	SWAP	0x70
0x5	SUB 0xD	0x4D
0x6	SWAP	0x70
0x7	JNZ 0x3	0x83

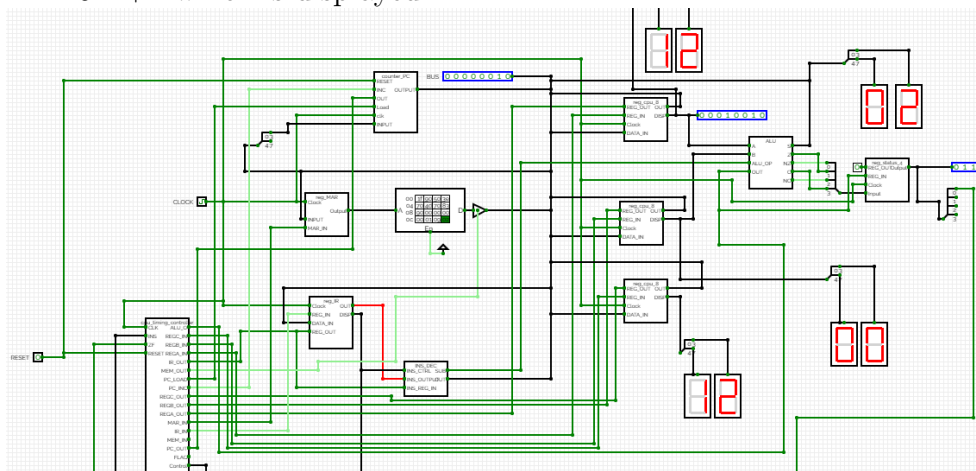Consider  $9 * 2$  9 is stored in location in location  $0xE$  and 2 in location  $0xF$ . The output is  $12 = 16 * 1 + 2$  which is displayed.



## 4 MICROINSTRUCTIONS AND CONTROLLER LOGIC DESIGN

We define our own control word format. The size of the control word is up to our design. We have taken size of control word as 16.

We can do this controller both hardware and software based. As of now, we have made a software design. We have to use a fixed number of T-states for all instructions to keep the design simple. Here, we use 5 T-states.

The control unit is the key to the operations formed. The control unit generates the control words that fetch and execute each instruction. While each instruction is fetched and executed, it passes through different timing states (T-states). We take 5 T-states (two fetch and three execute). These five states are called a machine cycle.

For each instruction, we define the sequence of microinstructions or control words that need to be executed in sequence which are given below:

### 4.1 NOP

```
T0:  1<<PC_OUT  | 1<<MAR_IN
T1:  1<<PC_INC   | 1<<MEM_OUT  | 1<<IR_IN
T2:  0
T3:  0
T4:  0
```

The minimum number of T-states : 3

### 4.2 LDA

```
T0:  1<<PC_OUT  | 1<<MAR_IN
T1:  1<<PC_INC   | 1<<MEM_OUT  | 1<<IR_IN
T2:  1<<IR_OUT   | 1<<MAR_IN
T3:  1<<MEM_OUT  | 1<<REGA_IN
T4:  0
```

The minimum number of T-states : 4

### 4.3 STA

```
T0:  1<<PC_OUT  | 1<<MAR_IN
T1:  1<<PC_INC   | 1<<MEM_OUT  | 1<<IR_IN
T2:  1<<IR_OUT   | 1<<MAR_IN
```

T3: 1<<MEM\_IN | 1<<REGA\_OUT  
T4: 0

The minimum number of T-states : 4

#### 4.4 ADD

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<IR\_OUT | 1<<MAR\_IN  
T3: 1<<MEM\_OUT | 1<<REGB\_IN  
T4: 1<<ALU\_OUT | 1<<REGA\_IN

The minimum number of T-states : 5

#### 4.5 SUB

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<IR\_OUT | 1<<MAR\_IN  
T3: 1<<MEM\_OUT | 1<<REGA\_IN  
T4: 1<<ALU\_OUT | 1<<REGA\_IN

The minimum number of T-states : 5

#### 4.6 JMP

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<PC\_LOAD | 1<<IR\_OUT  
T3: 0  
T4: 0

The minimum number of T-states : 3

#### 4.7 SWAP

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGA\_OUT | 1<<REGB\_IN  
T3: 1<<REGA\_IN | 1<<REGC\_OUT  
T4: 1<<REGB\_OUT | 1<<REGC\_IN

The minimum number of T-states : 5

## 4.8 JNZ

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<PC\_LOAD | 1<<IR\_OUT  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.9 MOVAC

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGA\_OUT | 1<<REGC\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.10 MOVAC

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGA\_OUT | 1<<REGC\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.11 MOVBA

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGB\_OUT | 1<<REGA\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.12 MOVCB

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGC\_OUT| 1<<REGB\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.13 MOVAB

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGA\_OUT| 1<<REGB\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.14 MOVCA

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGC\_OUT| 1<<REGA\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 4.15 MOVBC

T0: 1<<PC\_OUT | 1<<MAR\_IN  
T1: 1<<PC\_INC | 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<REGB\_OUT| 1<<REGC\_IN  
T3: 0  
T4: 0

The minimum number of T-states : 3



## 4.16 HLT

T0: 1<<MAR\_IN  
T1: 1<<MEM\_OUT | 1<<IR\_IN  
T2: 1<<FLAG  
T3: 0  
T4: 0

The minimum number of T-states : 3

## 5 SYSTEM RESET

A system reset typically refers to a process where a circuit is brought back to its initial state or starting point. During this reboot, the processor's program counter is set to 0x0, and internal counters within the system are reset to their initial states. It involves three steps

- 1) Set RESET to 1
- 2) Toggle the clock
- 3) Set RESET to 0